



**Politechnika
Śląska**

Filtry pasywne

Jacek Izydorczyk


25.04.2023 r.

.....dla inżyniera elektryka mniej ważne jest rozwiązywanie zadanych równań różniczkowych niż poszukiwanie układów równań różniczkowych (obwodów), których rozwiązanie ma pożądaną właściwość...


Wilhelm Adolf Eduard Cauer
Theorie der linearen Wechselstromschaltungen

- sformułowanie problemu
- filtry pseudoeliptyczne
- od parametrów S do parametrów Y
- filtr prototypowy
- przekształcenia
- wnioski

Sformułowanie problemu 1

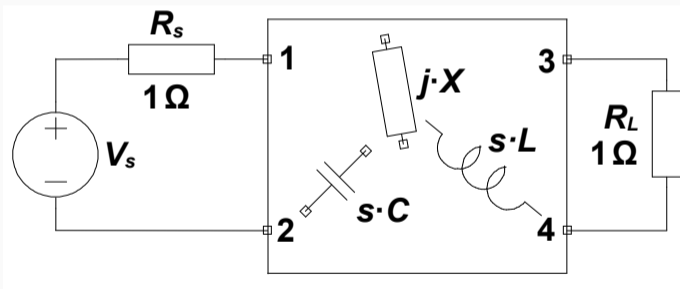


Sformułowanie problemu 2

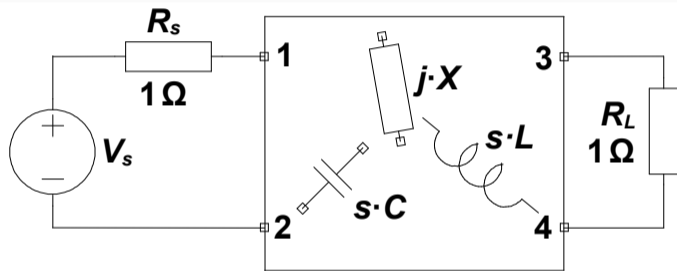

$$S_{12}^2(\Omega) = \left| \frac{2V(3,4)}{V_s} \right|^2 = \frac{1}{1 + \varepsilon^2 F^2(\Omega)}$$

Sformułowanie problemu 3

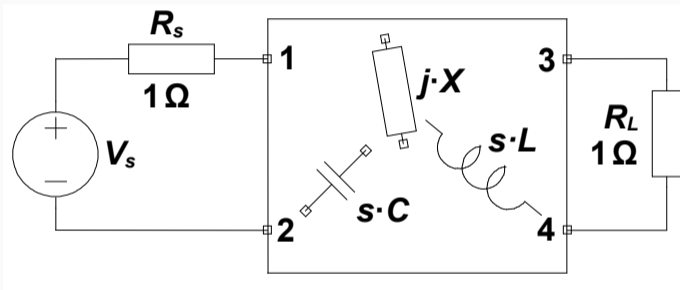


$$S_{12}^2(\Omega) = \frac{1}{1 + \varepsilon^2 F^2(\Omega)} \Rightarrow S_{11}^2(\Omega) = \frac{\varepsilon^2 F^2(\Omega)}{1 + \varepsilon^2 F^2(\Omega)}$$


Funkcja charakterystyczna

$$F(\Omega) = C_N(\Omega) = \cosh \left(\sum_{n=1}^N \cosh^{-1} \left(\frac{\Omega - 1/\Omega_n}{1 - \Omega/\Omega_n} \right) \right).$$
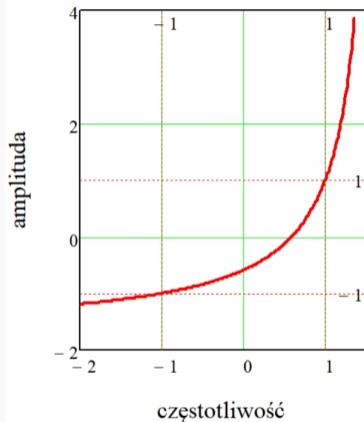
$$F(\Omega) = T_N(\Omega) = \cosh \left(\sum_{n=1}^N \cosh^{-1}(\Omega) \right).$$



Filtr pseudoeliptyczny vs. Butterwortha

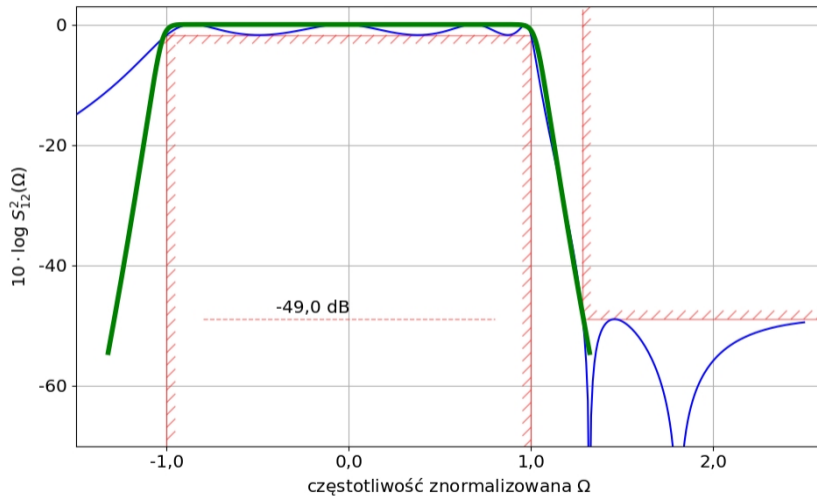

Obliczanie $C_N(\Omega)$

$$\cosh^{-1}(x) = \ln(x + \sqrt{x^2 - 1}),$$

$$C_N(\Omega) = \cosh\left(\sum_{n=1}^N \ln(x_n + \sqrt{x_n^2 - 1})\right),$$

gdzie: $x_n = (\Omega - 1/\Omega_n)/(1 - \Omega/\Omega_n)$.

$$C_N(\Omega) = \frac{1}{2} \left(\underbrace{\prod_{n=1}^N (x_n + \sqrt{x_n^2 - 1})}_{W_N(x_n) + P_N(x_n)\sqrt{x_n^2 - 1}} + \prod_{n=1}^N (x_n - \sqrt{x_n^2 - 1}) \right).$$

Obliczanie $C_N(\Omega)$ – finał

$$C_N(\Omega) = \frac{F_N(\Omega)}{D_N(\Omega)}$$

$$D(\Omega) = \prod_{n=1}^N \left(1 - \Omega/\Omega_n\right).$$

$$\frac{\boxed{F_n(\Omega)}}{\boxed{V_n(\Omega)}} = \frac{\boxed{\Omega - \frac{1}{\Omega_n}} \quad \boxed{(\Omega^2 - 1)\sqrt{1 - \frac{1}{\Omega_n^2}}}}{\boxed{\sqrt{1 - \frac{1}{\Omega_n^2}}} \quad \boxed{\Omega - \frac{1}{\Omega_n}}} \cdot \frac{\boxed{F_{n-1}(\Omega)}}{\boxed{V_{n-1}(\Omega)}}.$$

$$F_0(\Omega) = 1 \quad V_0(\Omega) = 0.$$

Wzór rekurencyjny

$$F_n(\Omega) = \left(\Omega - \frac{1}{\Omega_n}\right)F_{n-1}(\Omega) + \\ + \left(\Omega - \frac{1}{\Omega_{n-1}}\right)\sqrt{\frac{1 - 1/\Omega_n^2}{1 - 1/\Omega_{n-1}^2}}F_{n-1}(\Omega) - \\ - \left(1 - \frac{\Omega}{\Omega_{n-1}}\right)^2\sqrt{\frac{1 - 1/\Omega_n^2}{1 - 1/\Omega_{n-1}^2}}F_{n-2}(\Omega)$$

Obliczanie $S_{12}(s)$ i $S_{11}(s)$

$$S_{11}(s) = \frac{Q(s)}{E(s)}, \quad S_{21}(s) = \frac{P(s)}{\varepsilon E(s)},$$

$$P(s) = (-j)^K \prod_{k=1}^K (s - j \cdot \Omega_k). \quad Q(s) = (-j)^N \prod_{n=1}^N (s - j \cdot \underbrace{\Omega'_n}_{F_N(\Omega'_n)=0}),$$

$$\varepsilon = \left| \frac{Q(s)}{P(s)} \right|_{s=\pm j} \frac{1}{\sqrt{10^{0,1 \cdot RL} - 1}},$$

Obliczanie $S_{12}(s)$ i $S_{11}(s)$ cd

$$\{e_n : \Re(r_n) < 0 \text{ oraz } P^2(e_k)/\varepsilon^2 + Q^2(e_k) = 0\}$$

$$E(s) = \varepsilon_R \prod_{n=1}^N (s - e_n),$$

natomiast:

$$\varepsilon_R = \begin{cases} 1 & \text{gdy } K < N, \\ \frac{\varepsilon}{\sqrt{\varepsilon^2 - 1}} & \text{gdy } K = N. \end{cases}$$

$$S \mapsto Y$$

$$Y_{\text{in}}(s) = \frac{1 - S_{11}(s)}{1 + S_{11}(s)} = \frac{E(s) - Q(s)}{E(s) + Q(s)}.$$

$$n_1(s) = \text{Re}[\text{Ev}(E - Q)] + j \cdot \text{Im}[\text{Odd}(E - Q)],$$

$$m_1(s) = \text{Re}[\text{Odd}(E - Q)] + j \cdot \text{Im}[\text{Ev}(E - Q)],$$

$$n_2(s) = \text{Re}[\text{Ev}(E + Q)] + j \cdot \text{Im}[\text{Odd}(E + Q)],$$

$$m_2(s) = \text{Re}[\text{Odd}(E + Q)] + j \cdot \text{Im}[\text{Ev}(E + Q)].$$

$S \mapsto Y \quad \mathbf{cd}$

$$y_{11}(s) = \begin{cases} \frac{m_2(s)}{n_2(s)} & \text{gdy } N \text{ jest parzyste,} \\ \frac{n_2(s)}{m_2(s)} & \text{gdy } N \text{ jest nieparzyste,} \end{cases}$$

$$y_{22}(s) = \begin{cases} \frac{m_2(s)}{n_2(s)} & \text{gdy } N \text{ jest parzyste,} \\ \frac{n_1(s)}{m_2(s)} & \text{gdy } N \text{ jest nieparzyste,} \end{cases}$$

$$y_{12}(s) = y_{21}(s) = \begin{cases} \frac{j \cdot P(s)}{\varepsilon \cdot n_2(s)} & \text{gdy } N \text{ jest parzyste,} \\ \frac{P(s)}{\varepsilon \cdot m_2(s)} & \text{gdy } N \text{ jest nieparzyste.} \end{cases}$$

-  Wilhelm A.E. Cauer.
Theorie der linearen Wechselstromschaltungen.
Akademische Verlagsgesellschaft Becker & Erler Kom.-Ges., Leipzig, 1941.
-  J. L. Herrero and G. Willoner.
Synthesis of Filters.
Prentice-Hall, Inc., Englewood Cliffs, New Jersey, 1966.

Niezmiennik

$$n_1(s) \cdot n_2(s) - m_1(s) \cdot m_2(s) = P^2(s)/\varepsilon^2.$$

Niezmiennik cd

$$y_{11}(s) \cdot y_{22}(s) - 1 = y_{21}^2(s).$$

$$r_{11_n} \cdot r_{22_n} = r_{21_n}^2 \quad \text{dla } n = 1, \dots, N.$$

Filtry parzystego rzędu – S_{11}

$$Y_{\text{in}} = \frac{y_{11} + y_{22} \cdot y_{11} - y_{12} \cdot y_{21}}{1 + y_{22}}.$$

$$y_{11}(s) = \frac{m_2(s)}{n_2(s)}, \quad y_{22}(s) = \frac{m_1(s)}{n_2(s)} = y_{11}(s), \quad y_{12}(s) = y_{21}(s) = \frac{jP(s)/\varepsilon}{n_2(s)}.$$

$$Y_{\text{in}} = \frac{\frac{m_2}{n_2} + \overbrace{\frac{m_1 m_2}{n_2^2} + \frac{P^2/\varepsilon^2}{n_2^2}}^{\uparrow}}{1 + \frac{m_1}{n_2}} = \frac{\frac{m_2}{n_2} + \overbrace{\frac{n_1 n_2}{n_2^2}}^{\downarrow}}{1 + \frac{m_1}{n_2}} = \frac{m_1 + n_1}{n_2 + m_2} = \frac{E - Q}{E + Q}$$


Filtry parzystego rzędu – S_{12}

$$K_u = \frac{-y_{21}}{(1 + y_{22}) + y_{11} + y_{22} \cdot y_{11} - y_{21} \cdot y_{21}}$$

$$\begin{aligned} K_u &= \frac{-jP/\varepsilon/n_2}{1 + \frac{m_1}{n_2} + \frac{m_2}{n_2} + \underbrace{\frac{m_1 m_2}{n_2^2} + \frac{P^2/\varepsilon^2}{n_2^2}}_{\rightarrow}} = \\ &= \frac{-jP/\varepsilon/n_2}{1 + \frac{m_1}{n_2} + \frac{m_2}{n_2} + \underbrace{\frac{n_1 n_2}{n_2^2}}_{\rightarrow}} = \frac{-jP/\varepsilon}{n_1 + m_1 + n_2 + m_2} = \frac{-jP/\varepsilon}{2E}. \end{aligned}$$


Obwód prototypowy – wejście
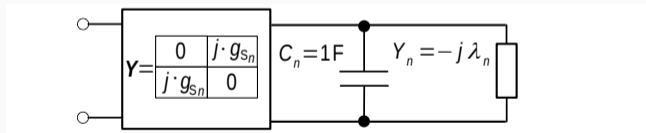
$$y_{11}(s) = r_{11_0} + \sum_{n=1}^N \frac{r_{11_n}}{s - j \cdot \lambda_n}, \quad \text{gdzie } r_{11_n} > 0 \quad \text{dla } n = 1, \dots, N.$$



$$g_{S_n} = \sqrt{r_{11_n}}.$$


Obwód prototypowy – we. i wy.

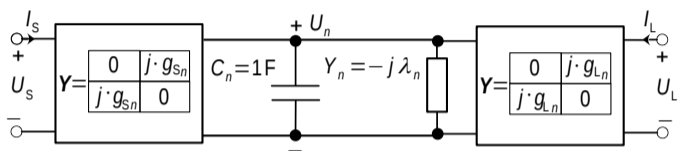


$$g_{S_n} = \sqrt{r_{11_n}}, \quad g_{L_n} = \frac{r_{21_n}}{\sqrt{r_{11_n}}} = \sqrt{r_{22_n}}.$$


$$y_{11_n} = \frac{r_{11_n}}{s - j \cdot \lambda_n}, \quad y_{22_n} = \frac{r_{22_n}}{s - j \cdot \lambda_n}, \quad y_{21_n} = y_{12_n} = \frac{r_{21_n}}{s - j \cdot \lambda_n}.$$

Przykład 1/5

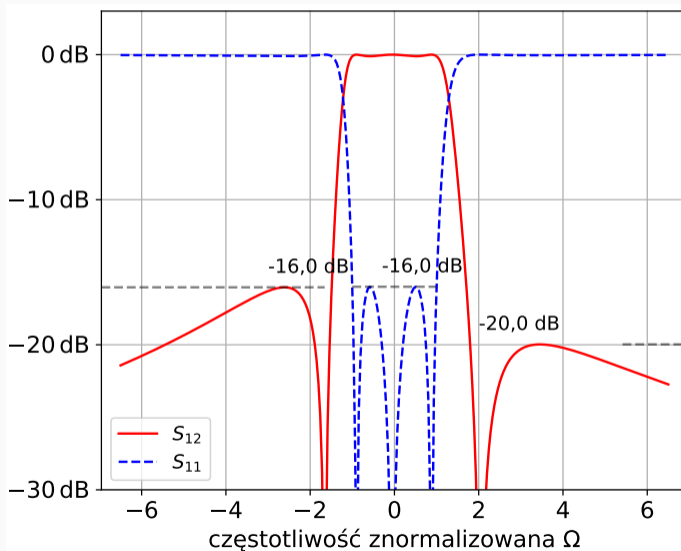


Przykład 2/5

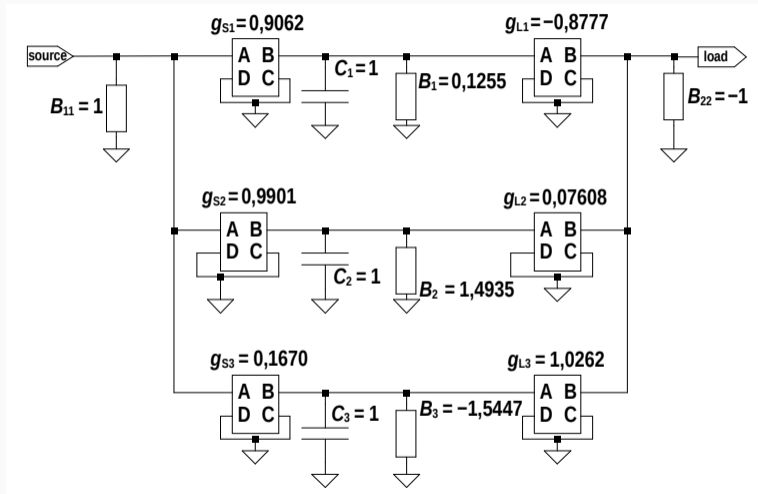

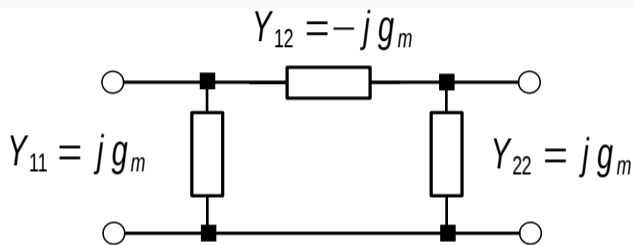



$$Y = \begin{pmatrix} jg_m - jg_m & -jg_m \\ -jg_m & jg_m - jg_m \end{pmatrix} = \begin{pmatrix} 0 & -jg_m \\ -jg_m & 0 \end{pmatrix}.$$

Przykład 3/5

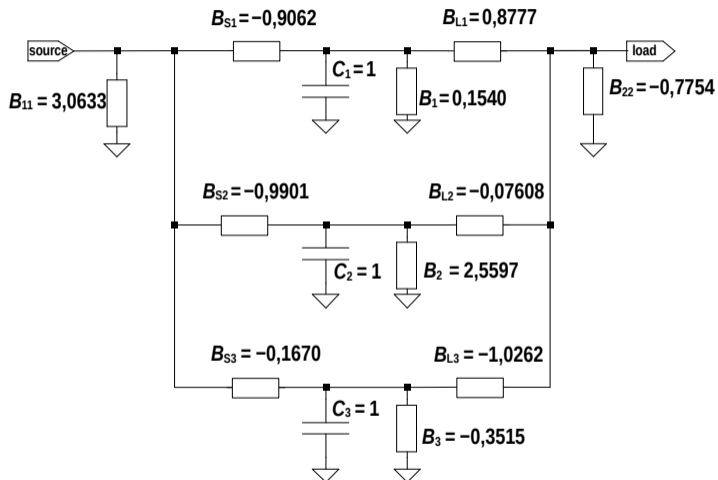

LTSpice 1/3

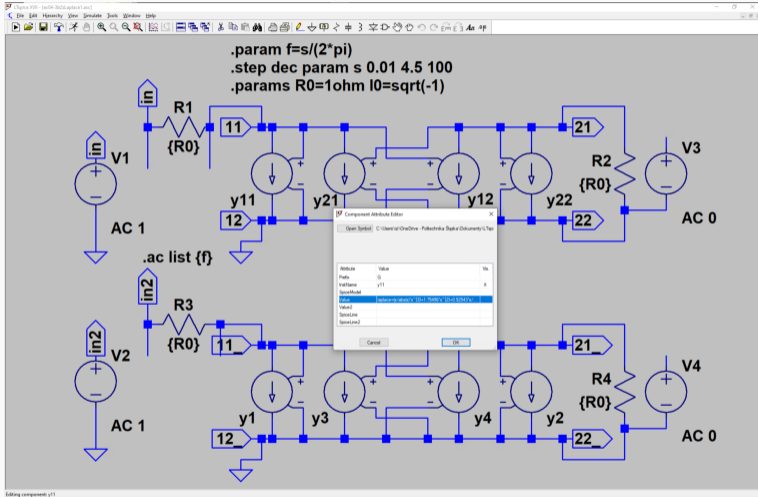

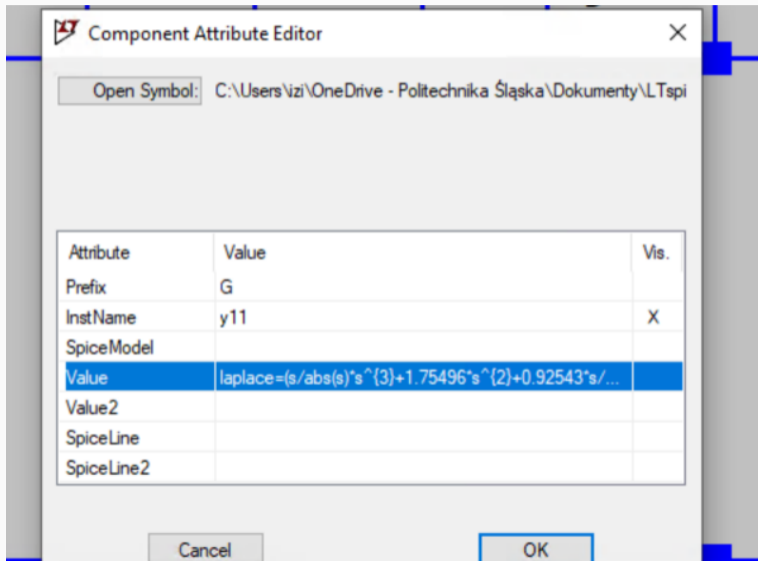

LTSpice 3/3

The screenshot displays four windows from the LTSpice software interface:

- Top-left window:** A circuit diagram with a resistor $R1$ (value $\{R_{xxx}\}$) in parallel with a capacitor $C1$ (value $\{1/R\}$). The circuit is connected between terminals 1 and 2. Below the circuit, the parameter definition is given as `.param R=1 Rxxx=1G`.
- Top-right window:** A circuit diagram showing a resistor $R1$ connected between terminals 1 and 2. The transfer function is indicated as $\{-1/B\}$.
- Bottom-left window:** A complex circuit diagram titled "Analiza pseudo AC Filtru Czebyszewa" (Pseudo AC Filter Chebyshev Analysis). It features an AC voltage source $V1$, a resistor $xR1$, and a network of dependent current sources (xM), capacitors (C), and resistors (xR). The circuit is connected to an AC ground $AC 0$. The analysis parameters are: `.param s=-1`, `.ac lin (10)wj`, and `.stop param e -6.5 6.5 0.01`.
- Bottom-right window:** A circuit diagram showing a resistor $R1$ connected between terminals 1 and 2. The transfer function is indicated as $\{-1/s/C\}$.


$$Y(s) = sE + j \cdot M \quad E = \text{diag}(0, 1, \dots, 1, 0)$$

$$M = \begin{array}{cccccccccc}
B_{11} & g_{S1} & g_{S2} & g_{S3} & \cdots & g_{Sn} & \cdots & g_{SN-1} & g_{SN} & g_{SL} \\
g_{S1} & B_1 & 0 & 0 & \cdots & 0 & \cdots & 0 & 0 & g_{L1} \\
g_{S2} & 0 & B_2 & 0 & \cdots & 0 & \cdots & 0 & 0 & g_{L2} \\
g_{S3} & 0 & 0 & B_3 & \cdots & 0 & \cdots & 0 & 0 & g_{L3} \\
\vdots & \vdots & \vdots & \vdots & \ddots & \vdots & \ddots & \vdots & \vdots & \vdots \\
g_{Sn} & 0 & 0 & 0 & \cdots & B_n & \cdots & 0 & 0 & g_{Ln} \\
\vdots & \vdots & \vdots & \vdots & \ddots & \vdots & \ddots & \vdots & \vdots & \vdots \\
g_{SN-1} & 0 & 0 & 0 & \cdots & 0 & \cdots & B_{N-1} & 0 & g_{LN-1} \\
g_{SN} & 0 & 0 & 0 & \cdots & 0 & \cdots & 0 & B_N & g_{LN} \\
g_{SL} & g_{L1} & g_{L2} & g_{L3} & \cdots & g_{Ln} & \cdots & g_{LN-1} & g_{LN} & B_{22}
\end{array}$$

Przykład 4/5

$$M =$$

	S	1	2	3	L	
	1,00	0,91	0,99	0,17	0	S
	0,91	0,13	0	0	-0,88	1
	0,99	0	1,49	0	0,08	2
	0,17	0	0	-1,54	1,03	3
	0	-0,88	0,08	1,03	-1,00	L

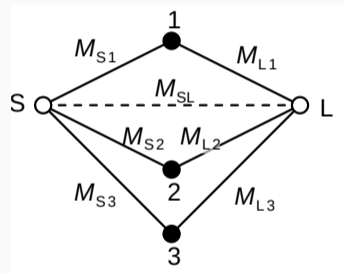


$$Y \mapsto RYR^{-1}.$$


$$R(i, j, \varphi) = \begin{array}{ccccccc} 1 & & & & & & \\ & \ddots & & & & & \\ & & 1 & & & & \\ & & & \cos \varphi & \cdots & & -\sin \varphi & \cdots & i \\ & & & & 1 & & & & \\ & & & \vdots & & \ddots & & \vdots & \\ & & & & & & 1 & & \\ & & & \sin \varphi & \cdots & & & \cos \varphi & \cdots & j \\ & & & \vdots & & & & \vdots & & \\ & & & & & & & & & \\ & & & i & & & & j & & \end{array}$$

Przykład 5/5
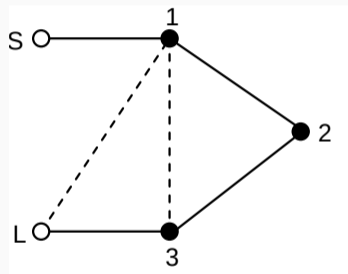
$$M''' = \begin{pmatrix} 1 & 1,35 & 0 & 0 & 0 \\ 1,35 & 0,83 & 0,73 & 0,12 & -0,41 \\ 0 & 0,73 & 0,16 & 0,99 & 0 \\ 0 & 0,12 & 0,99 & -0,92 & 1,29 \\ 0 & -0,41 & 0 & 1,29 & -1 \end{pmatrix}$$




Filtr Czebyszewa 1/4

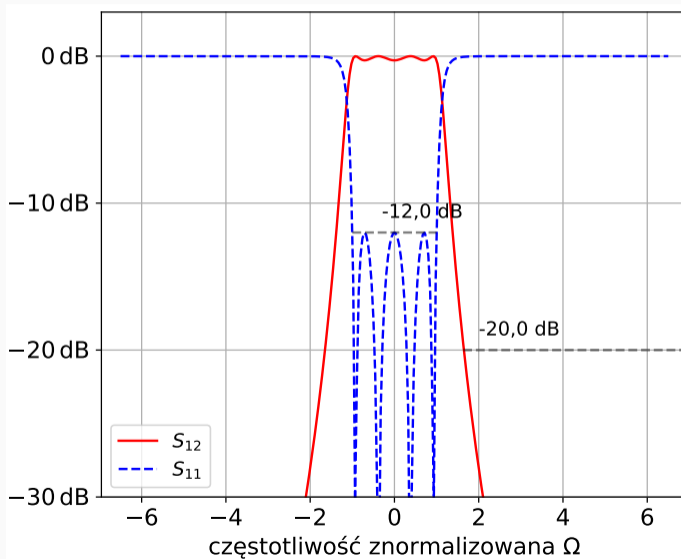


$$M = \begin{pmatrix} 0 & 0,492 & 0,492 & 0,33 & 0,33 & 0 \\ 0,492 & 0,5 & 0 & 0 & 0 & -0,492 \\ 0,492 & 0 & -0,5 & 0 & 0 & 0,492 \\ 0,33 & 0 & 0 & -1,115 & 0 & -0,33 \\ 0,33 & 0 & 0 & 0 & 1,115 & 0,33 \\ 0 & -0,492 & 0,492 & -0,33 & 0,33 & 0 \end{pmatrix}.$$

Filtr Czebyszewa 3/4

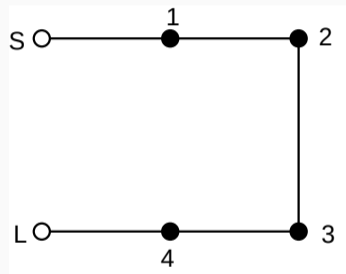
$$M = \begin{pmatrix} 0 & 0,838 & 0 & 0 & 0 & 0 \\ 0,838 & 0 & 0,747 & 0 & 0 & 0 \\ 0 & 0,747 & 0 & -0,614 & 0 & 0 \\ 0 & 0 & -0,614 & 0 & -0,747 & 0 \\ 0 & 0 & 0 & -0,747 & 0 & 0,838 \\ 0 & 0 & 0 & 0 & 0,838 & 0 \end{pmatrix}$$




Filtr Czebyszewa 4/4

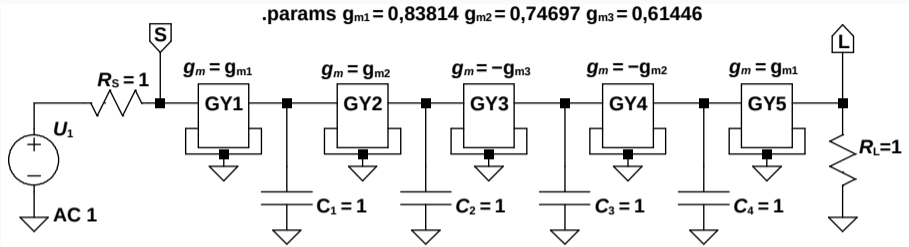

a)

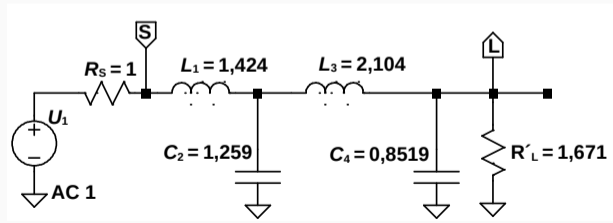


b)

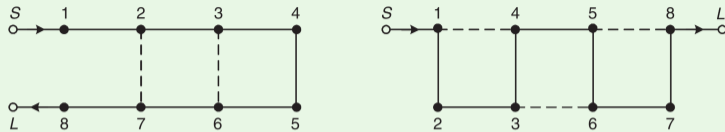

(a)

(b)

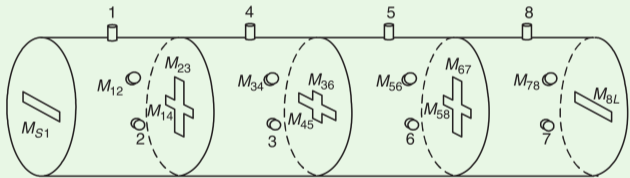


Physical Cavity No.		1	2	3	4
Containing Electrical Resonance Numbers	Vertical Polarization	1	4	5	8
	Horizontal Polarization	2	3	6	7

(c)

$$\Delta\alpha = 20 \log_{10} \left(\frac{S(0)}{S(0) + \Delta S(0)} \right) \approx \frac{20}{\ln 10} \frac{\beta \cdot T(0)}{Q}.$$

Rezonatory

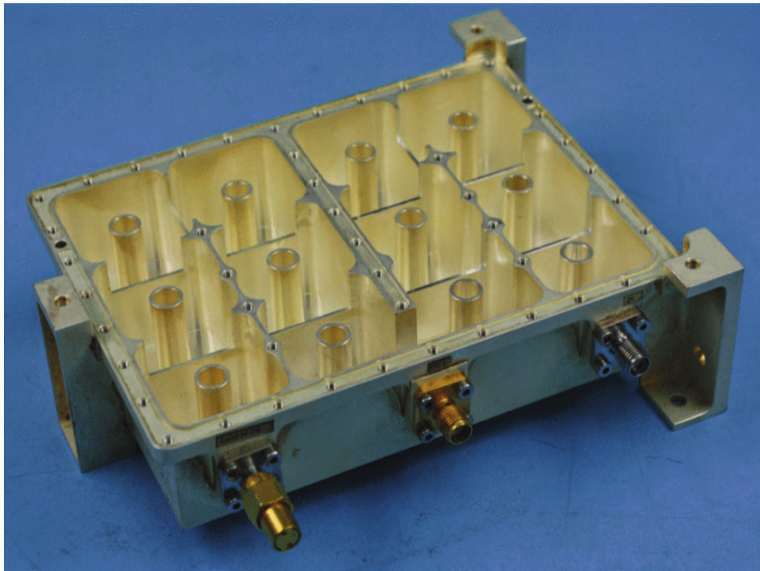

Filtry pasywne



: (